




YAKIN DOĞU ÜNİVERSİTESİ
UZAKTAN EĞİTİM VE BİLİŞİM TEKNOLOJİLERİ MERKEZİ


EE 471 POWER SYSTEM ANALYSIS I

Prof. Dr. Sezai Dinçer

OUTLINES 1

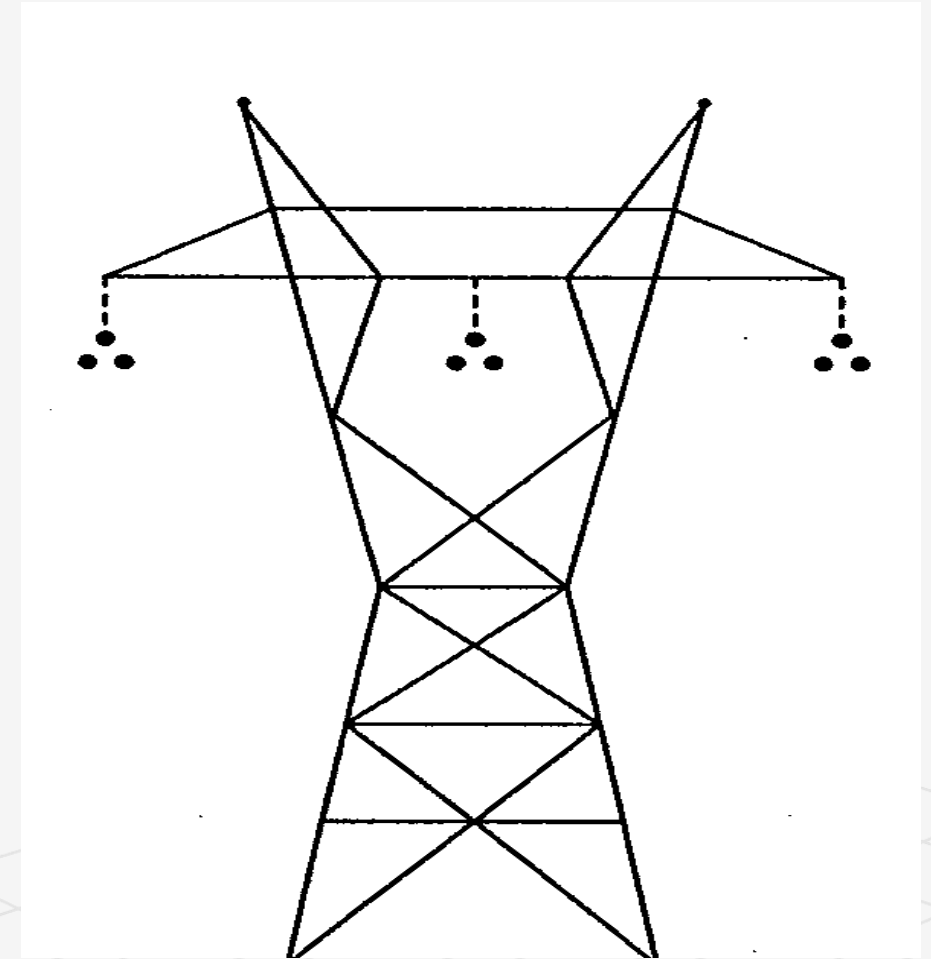


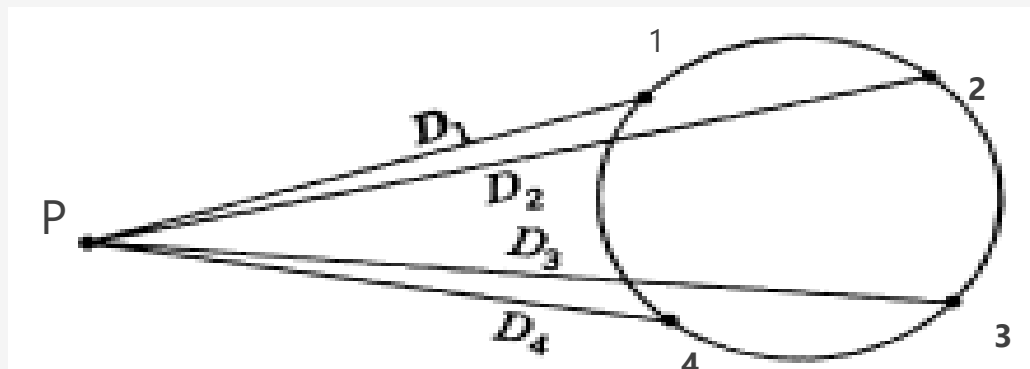INDUCTANCE AND CAPACITANCE CALCULATIONS AND GMD



$$GMD = \sqrt[4]{D_1 D_2 D_3 D_4}$$

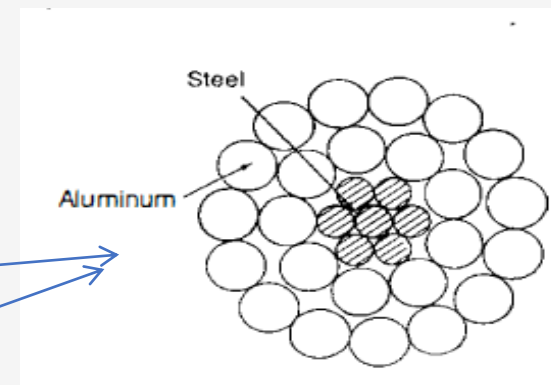
$$L = 2 \times 10^{-7} \ln \frac{D_m}{D_s} \text{ henrys/meter}$$




$$C_{an} = \frac{2\pi\epsilon}{\ln(D_{eq}/r)} \text{ F/m}$$

$$D_{eq} = \sqrt[3]{D_{ab} D_{bc} D_{ac}}$$

54/7 Cardinal

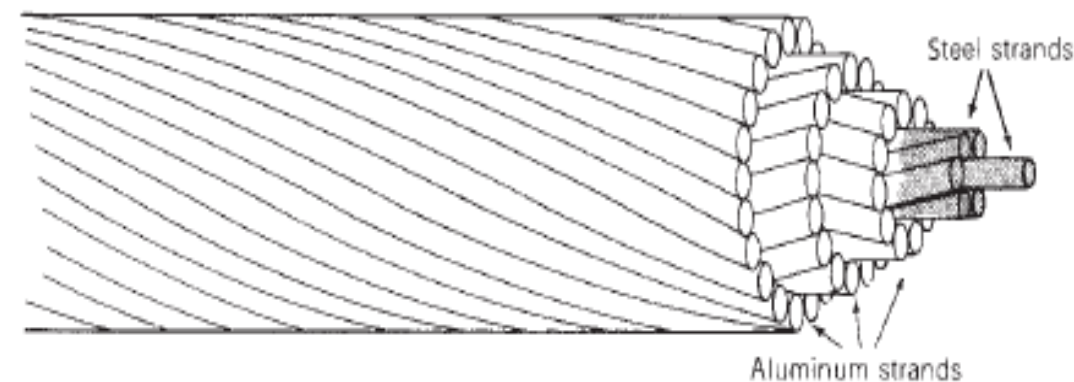

Self GMD (GMR)

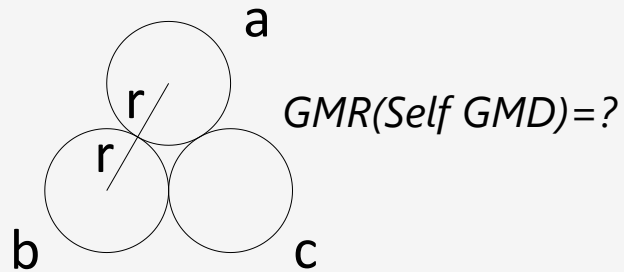


$$GMR = (D_{aa}D_{ab}D_{ac}D_{bb}D_{ba}D_{bc}D_{cc}D_{ca}D_{cb})^{1/9}$$

$$GMR = (0.7788r \times 2r \times 2r \times 0.7788r \times 2r \times 2r \times 0.7788r \times 2r \times 2r)^{1/9}$$

$$GMR = (0.7788r \times 2r \times 2r)^{1/3} = 1.46r$$

EXAMPLE

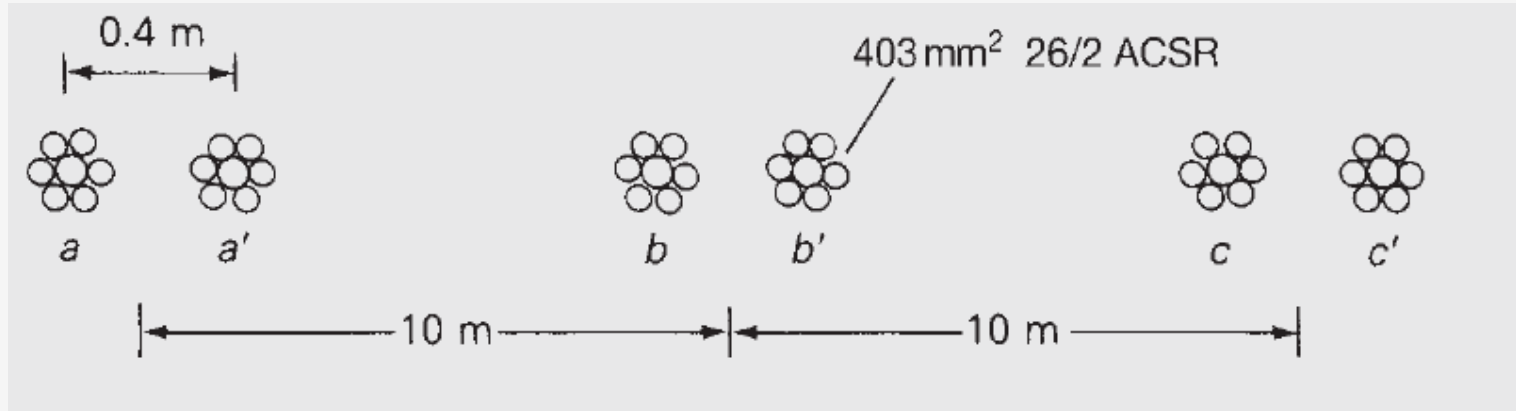

3 Phase Line with bundle conductors. SGMR of stranded conductor is 0.0114 m .

Line is transposed. Calculate the line inductance.. (f=60 Hz, I =200 km))

$$D_{eq} = \sqrt[3]{(10)(10)(20)} = 12.6 \text{ m}$$

$$D_{SL} = \sqrt{(0.0114)(0.40)} = 0.0676 \text{ m}$$

$$L_a = 2 \times 10^{-7} \ln \left(\frac{12.6}{0.0676} \right) (1000)(200) = 0.209 \text{ H}$$

$$X_a = 2\pi f L_1 = (2\pi)(60)(0.209) = 78.8 \text{ } \Omega$$

BUNDLED CONDUCTORS

Two-conductor bundle:

$$D_{SL} = \sqrt[4]{(D_S \times d)^2} = \sqrt{D_S d}$$


Three-conductor bundle:

$$D_{SL} = \sqrt[9]{(D_S \times d \times d)^3} = \sqrt[3]{D_S d^2}$$


Four-conductor bundle:

$$D_{SL} = \sqrt[16]{(D_S \times d \times d \times d \sqrt{2})^4} = 1.091 \sqrt[4]{D_S d^3}$$


TWO CONDUCTOR

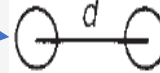


THREE CONDUCTOR

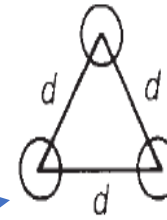

FOUR CONDUCTOR

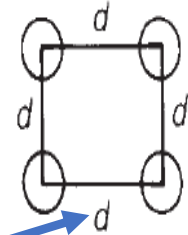


TUTORIAL

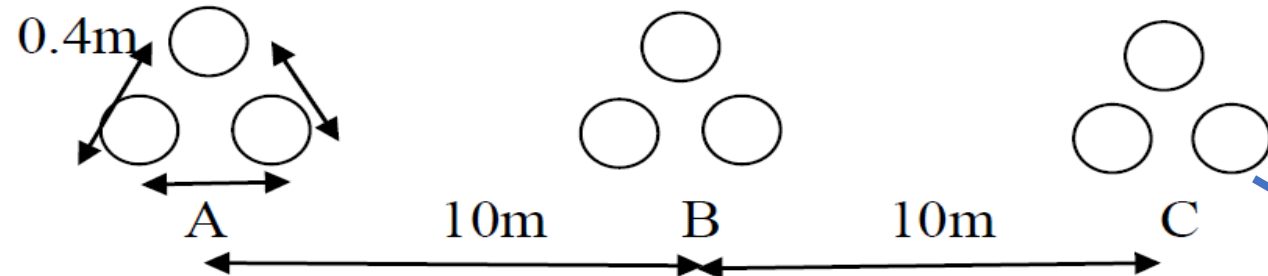

Three phase, 50 Hz transmission line with three conductor bundles. Assume that sub conductor is solid round with $r = 1.8$ cm. The line is completely transposed.

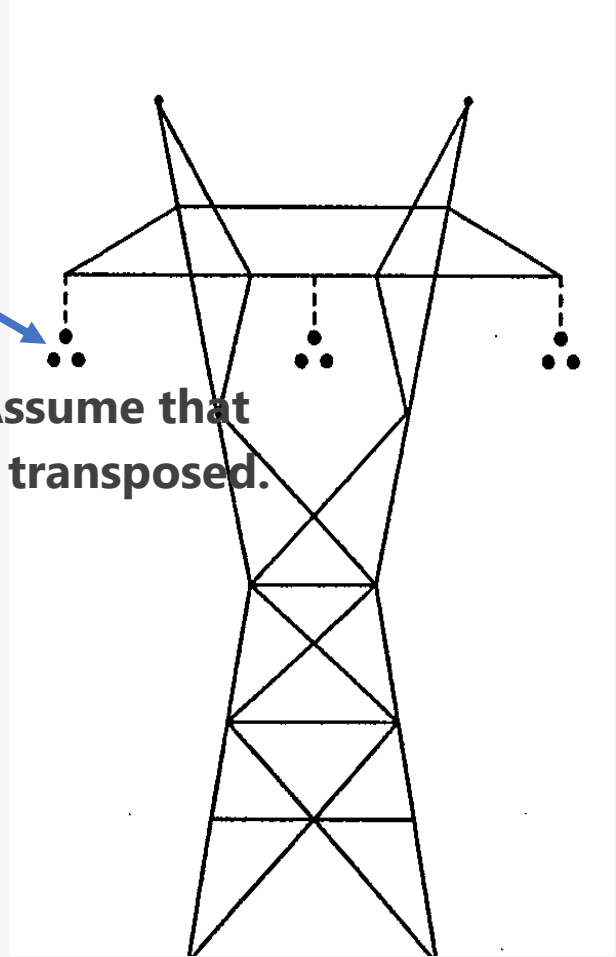- Find the inductance per phase per unit length.
- If the line is a 350 km line calculate the line reactance per phase.



SOLUTION

a)

$$D_S = (r^1 \times 0.4 \times 0.4 \times r^1 \times 0.4 \times 0.4 \times r^1 \times 0.4 \times 0.4)^{1/9}$$
$$r^1 = 0.7788 \times 1.8 \times 10^{-2} \text{ m}$$
$$D_S = 0.13 \text{ m}$$

$$D_m = (D_{AB} D_{AC} D_{BC})^{1/3}, \quad D_m = 12.6 \text{ m}$$

$$L = 2 \times 10^{-7} \ln (D_m / D_S) \text{ H/m per phase}$$
$$L = 9.133 \times 10^{-7} \text{ H/m per phase}$$

b)

$$X = j (2\pi \times 50) \times 9.133 \times 10^{-7} \times 350000 = j 100.4 \text{ ohm}$$

LINE MODELS

SHORT LINE

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$A = D = 1$$

$$B = Z \quad \Omega$$

$$C = 0 \quad S$$

MEDIUM LENGTH

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} \left(1 + \frac{YZ}{2}\right) & Z \\ Y\left(1 + \frac{YZ}{4}\right) & \left(1 + \frac{YZ}{2}\right) \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$A = D = 1 + \frac{YZ}{2}$$

$$B = Z \quad \Omega$$

$$C = Y \left(1 + \frac{YZ}{4}\right)$$

LONG LINE

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$A = D = \cosh(\gamma l)$$

$$B = Z_c \sinh(\gamma l) \quad \Omega$$

$$C = \frac{1}{Z_c} \sinh(\gamma l) \quad S$$

LONG LINE

$$V(x) = \left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) V_R + Z_c \left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right) I_R$$

$$I(x) = \frac{1}{Z_c} \left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right) V_R + \left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) I_R$$

$$\cosh(\gamma l) = \frac{e^{\gamma l} + e^{-\gamma l}}{2} = \frac{1}{2} (e^{\alpha l} / \beta l + e^{-\alpha l} / -\beta l)$$

$$\sinh(\gamma l) = \frac{e^{\gamma l} - e^{-\gamma l}}{2} = \frac{1}{2} (e^{\alpha l} / \beta l - e^{-\alpha l} / -\beta l)$$

$$V(x) = V_R \cosh \gamma x + I_R Z_c \sinh \gamma x$$

$$I(x) = I_R \cosh \gamma x + \frac{V_R}{Z_c} \sinh \gamma x$$

$$V = \frac{V_R + I_R Z_c}{2} e^{\alpha x} e^{j\beta x} + \frac{V_R - I_R Z_c}{2} e^{-\alpha x} e^{-j\beta x}$$

$$I = \frac{V_R / Z_c + I_R}{2} e^{\alpha x} e^{j\beta x} - \frac{V_R / Z_c - I_R}{2} e^{-\alpha x} e^{-j\beta x}$$

Incident wave

Reflected wave

Propagation constant

$$\gamma = \alpha + j\beta \quad \text{m}^{-1}$$

The quantity γl is dimensionless. Also

$$e^{\gamma l} = e^{(\alpha + j\beta)l} = e^{\alpha l} e^{j\beta l} = e^{\alpha l} / \beta l$$

TUTORIAL PROBLEM

3 Phase, 50 Hz power transmission line has the following line parameters. Receiving end is unloaded with $V_r = 132$ KV.

- Determine the incident voltage wave at the receiving end.
- Determine the reflected voltage wave at the receiving end.
- Find the voltage at 120 km away from the receiving end.

$R = 0.2 \text{ ohm}, L = 1.3 \text{ mH}$ and $C = 0.01 \text{ } \mu\text{F}$ \longrightarrow Per km.

$$z = r + jx = (0.2 + j1.3 \times 314 \times 10^{-3}) = (0.2 + j0.408) \\ = 0.454 \angle 63.88^\circ$$

$$\text{shunt admittance} = j\omega C = j314 \times 0.01 \times 10^{-6} \\ = 3.14 \times 10^{-6} \angle +90^\circ$$

$$Z_c = \sqrt{\frac{z}{y}} = \sqrt{\frac{0.454}{0.314}} \times 10^5 \angle 63.88 - 90^\circ \\ = 380 \angle -13.06^\circ$$

$$\gamma = \sqrt{yz} = \sqrt{0.314 \times 0.454 \times 10^{-6}} \angle (90 + 63.88)^\circ / 2 \\ = (0.2714 + j1.169) \times 10^{-3} \\ = (\alpha + j\beta)$$

$$V_r = \frac{132 \times 1000}{\sqrt{3}} = 76200 \text{ volts}$$

Incident voltage wave
at the Receiving end

$$= \frac{V_r + I_r Z_c}{2}$$

$$I_r = 0.$$

$$\frac{V_r}{2} = \frac{76200}{2} = 38100 \text{ volts}$$

Reflected voltage wave
At the receiving end.

$$\frac{V_r - I_r Z_c}{2} = \frac{V_r}{2} = 38100 \text{ volts}$$

SOLUTION

Incident wave at

$$120 \text{ km.} = 38.1 \exp(0.2714 \times 120 \times 10^{-3}) \exp(j1.169 \times 120 \times 10^{-3})$$

$$= 39.35 \angle 8.02^\circ \text{ kV}$$

Reflected voltage

$$\text{Wave at 120 km} = 38.1 \exp(-\alpha x) \exp(-j\beta x) = 38.1 \exp(-0.0325) \exp(-j0.140)$$

$$= 36.88 \angle -8.02^\circ \text{ kV.}$$

Voltage at 120 km away from the receiving end is the summation of the voltage waves.

TUTORIAL

$$R = 0.2 \text{ ohm}, L = 1.3 \text{ mH and } C = 0.01 \text{ } \mu\text{F}$$

Km başına

$$\begin{aligned} z = r + jx &= (0.2 + j1.3 \times 314 \times 10^{-3}) = (0.2 + j0.408) \\ &= 0.454 \angle 63.88^\circ \end{aligned}$$

$$\begin{aligned} \text{shunt admittance} &= j\omega C = j314 \times 0.01 \times 10^{-6} \\ &= 3.14 \times 10^{-6} \angle +90^\circ \end{aligned}$$

$$\begin{aligned} Z_c &= \sqrt{\frac{z}{y}} = \sqrt{\frac{0.454}{0.314}} \times 10^5 \angle 63.88 - 90^\circ \\ &= 380 \angle -13.06^\circ \end{aligned}$$

$$\begin{aligned} \gamma &= \sqrt{yz} = \sqrt{0.314 \times 0.454 \times 10^{-6}} \angle (90 + 63.88)^\circ / 2 \\ &= (0.2714 + j1.169) \times 10^{-3} \\ &= (\alpha + j\beta) \end{aligned}$$

For the same line assume that 40 MW is transferred to The reciving end with pf 0.8 lag. If the receiving end is at 132 KV find the sending end voltage.

SOLUTION

$$I_r = \frac{40 \times 1000}{\sqrt{3} \times 132 \times 0.8}$$
$$= 218.7 \text{ amps.}$$

$$I_r = 218.7 \angle -36.8^\circ$$

$$e^{\alpha x} e^{j\beta x} = 1.033 \angle 8.02^\circ$$
$$e^{-\alpha x} e^{-j\beta x} = 0.968 \angle -8.02^\circ$$

For 120 kms.

$$V_s^+ = \frac{V_r + I_r Z_c}{2} e^{\alpha x} e^{j\beta x}$$
$$= \frac{76200 + 380 \times 218.7 \angle -13.06 \angle -36.8}{2} \times 1.033 \angle 8.02^\circ$$
$$= 74.63 \angle -18^\circ$$

$$V_s^- = \frac{V_r - I_r Z_c}{2} e^{-\alpha x} e^{-j\beta x}$$
$$= \frac{76200 - 380 \times 218.7 \angle -49.86}{2} \times 0.968 \angle -8.02^\circ$$
$$= 32.619 \angle 62.37 \text{ kV}$$

$$V_s = V_s^+ + V_s^- = 74.63 \angle -18^\circ + 32.619 \angle 62.37^\circ$$
$$= 86077 + j5751 = 86.26 \angle 3.82^\circ$$


TUTORIAL

Solve the same problem with nominal $-\pi$.

$$\text{Resistance} = 0.2 \times 120 = 24 \text{ ohms}$$

$$\text{Reactance} = 1.3 \times 10^{-3} \times 120 \times 314 = 48.98 \Omega$$
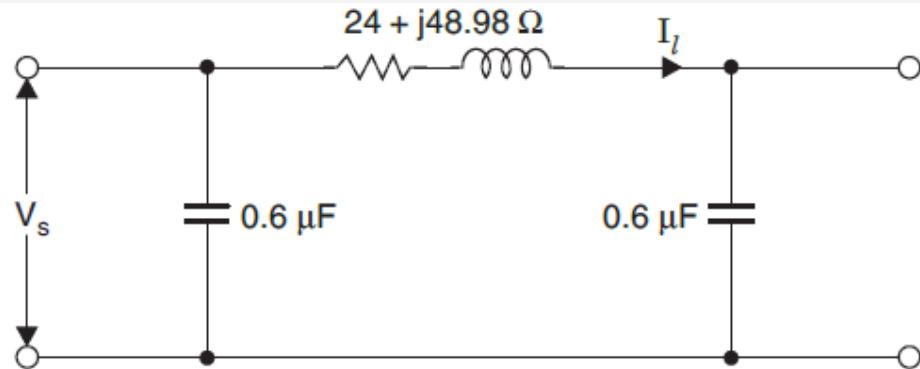
$$\text{Capacitance} = 0.01 \times 10^{-6} \times 120 = 1.2 \mu\text{F}$$



$$I_r = 218.7(0.8 - j0.6) = 174.96 - j131.22$$

$$I_{c_1} = j314 \times 0.6 \times 10^{-6} \times 76200 = j14.356 \text{ amp}$$

$$I_l = I_{c_1} + I_r = 174.96 - j116.86 = 210.39 \angle 33.73^\circ$$

$$\begin{aligned} V_s &= 76200 + (174.96 - j116.86)(24 + j48.38) \\ &= 76200 + 4199 + j8596 - j2804 + 5723 \\ &= 86122 + j5765 \\ &= 86314 \angle 3.82^\circ \text{ volts} \end{aligned}$$

TUTORIAL

3 phase , 50 Hz power line. Distances between phases are in order 3.7 , 6.475 and 7.4 meters. The line is completely transposed . Conductor SGMR = 0.978 cm.

$R = 0.1557$ ohm/km is defined per phase. 50 MVA is transferred at 0.8 pf lag with the receiving end voltage of 132 KV. Find V_s , I_s and A B C D line parameters.

SOLUTION

$$R = 0.1557 \times 160 = 24.9 \, \Omega$$

$$\begin{aligned} \text{GMD} &= \sqrt[3]{3.7 \times 6.475 \times 7.4} \\ &= 5.6 \text{ metre.} \end{aligned}$$

$$\begin{aligned} \text{Inductance} &= 2 \times 10^{-7} \left(\ln \frac{560}{0.978} \right) \times 160 \times 1000 \\ &= 0.2032 \text{ H} \end{aligned}$$

$$X_L = 63.8$$

$$\begin{aligned} C &= \frac{2\pi \epsilon_0}{\ln \frac{560}{0.978}} \times 160 \times 1000 \\ &= \frac{1}{36\pi} \times 10^{-9} \left(\frac{2\pi}{\ln \frac{560}{0.978}} \right) \times 160 \times 1000 \\ &= \frac{10^{-9}}{18} \times \frac{160000}{\ln \left(\frac{560}{0.978} \right)} \\ &= 1399 \times 10^{-9} \text{ F} \\ &= 1.399 \, \mu\text{F} \end{aligned}$$

$$Z = \sqrt{0.1557^2 + 0.39875^2} = 0.428 / \underline{68.67^\circ}$$

Solution

$$\begin{aligned}j\omega C &= j \times 314 \times \frac{1.399}{160} \times 10^{-6} \\ &= j 2.745 \times 10^{-6}\end{aligned}$$

$$\begin{aligned}Z_c &= \sqrt{\frac{0.428}{2.745} \times 10^{+6} / (68.67 - 90)} \\ &= 394.8 / -10.66^\circ\end{aligned}$$

$$\begin{aligned}\gamma &= \sqrt{0.428 \times 2.745 \times 10^{-6} / (90 + 68.67)} \\ &= 1.084 \times 10^{-3} / 79.335^\circ \\ &= (0.2 + j1.0653) \times 10^{-3}\end{aligned}$$

$$\begin{aligned}\gamma l &= (0.2 + j1.0653) \times 10^{-3} \times 160 \\ &= 0.0320 + j0.17\end{aligned}$$

$$\begin{aligned}A &= \cosh \gamma l = \cosh (0.032 + j0.17) \\ &= \cosh 0.032 \cos 0.17 + \sinh 0.032 \sin 0.17 \\ &= 0.9855 + j0.032 \times 0.16926 \\ &= 0.9855 + j0.005417 \\ &= 0.9855 / 0.32^\circ\end{aligned}$$

$$B = Z_c \sinh \gamma l$$

$$\begin{aligned}\sinh \gamma l &= \sinh 0.032 \cos 0.17 + j \cosh 0.032 \sin 0.17 \\ &= 0.032 \times 0.9835 + j0.9855 \times 0.17 \\ &= 0.0315 + j0.167535 \\ &= 0.17047 / 79.35^\circ\end{aligned}$$

$$\begin{aligned}B &= 394.8 \times 0.17047 / 79.35 - 10.66 \\ &= 67.3 / 68.69^\circ\end{aligned}$$

$$\begin{aligned}C &= \frac{\sinh \gamma l}{Z_c} = \frac{0.17047}{394.8} \\ &= 4.3 \times 10^{-4} / 90^\circ\end{aligned}$$

Solution

$$I_r = \frac{50,000}{\sqrt{3} \times 132} = 218.68 \text{ A}$$

$$\begin{aligned} V_s &= 0.9855/\underline{0.32^\circ} \times 76.208 + 67.3/\underline{68.69^\circ} \times 218.68/\underline{-36.87^\circ} \times 10^{-3} \\ &= 75.103/\underline{0.32^\circ} + 14.717/\underline{31.82^\circ} \\ &= 75.103 + 12.505 + j7.76 \\ &= 87.608 + j7.76 \end{aligned}$$

$$= 87.95/\underline{5.06^\circ}$$

$$V_s \text{ line to line} = 152.34 \text{ kV. } \mathbf{Ans.}$$

$$\begin{aligned} I_s &= 4.3 \times 10^{-4}/\underline{90^\circ} \times 76.208 \times 10^3 + 0.9855/\underline{0.32^\circ} \times 218.68/\underline{-36.87^\circ} \\ &= 32.76/\underline{90^\circ} + 215.51/\underline{-36.55^\circ} \\ &= j 32.76 + 173.12 - j 128.34 \\ &= 173.12 - j 95.58 \\ &= 197.75/\underline{-28.9^\circ}. \mathbf{Ans.} \end{aligned}$$