



YAKIN DOĞU ÜNİVERSİTESİ
UZAKTAN EĞİTİM VE BİLİŞİM TEKNOLOJİLERİ MERKEZİ

EE 471 POWER SYSTEM ANALYSIS I

Prof. Dr. Sezai Dinçer

LONG LINES II

LONG LINE EXPRESSIONS

$$V(x) = \left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) V_R + Z_c \left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right) I_R$$

$$I(x) = \frac{1}{Z_c} \left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right) V_R + \left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) I_R$$

$$\cosh(\gamma l) = \frac{e^{\gamma l} + e^{-\gamma l}}{2} = \frac{1}{2} (e^{\alpha l} / \beta l + e^{-\alpha l} / -\beta l)$$

$$\sinh(\gamma l) = \frac{e^{\gamma l} - e^{-\gamma l}}{2} = \frac{1}{2} (e^{\alpha l} / \beta l - e^{-\alpha l} / -\beta l)$$

$$V(x) = V_R \cosh \gamma x + I_R Z_c \sinh \gamma x$$

$$I(x) = I_R \cosh \gamma x + \frac{V_R}{Z_c} \sinh \gamma x$$

$$V = \frac{V_R + I_R Z_c}{2} e^{\alpha x} e^{j\beta x} + \frac{V_R - I_R Z_c}{2} e^{-\alpha x} e^{-j\beta x}$$

$$I = \frac{V_R / Z_c + I_R}{2} e^{\alpha x} e^{j\beta x} - \frac{V_R / Z_c - I_R}{2} e^{-\alpha x} e^{-j\beta x}$$

Incident wave

Reflected wave

Propagation constant

$$\gamma = \alpha + j\beta \quad \text{m}^{-1}$$

The quantity γl is dimensionless. Also

$$e^{\gamma l} = e^{(\alpha + j\beta)l} = e^{\alpha l} e^{j\beta l} = e^{\alpha l} / \beta l$$

Long Line Sending-Receiving end Current-Voltage Relationships

l : length of the line
 $x=l$,

$$V_S = V_R \cosh \gamma l + I_R Z_C \sinh \gamma l$$

$$I_S = I_R \cosh \gamma l + \frac{V_R}{Z_C} \sinh \gamma l$$


Therefore,

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$A = D = \cosh(\gamma l)$$

$$B = Z_c \sinh(\gamma l) \quad \Omega$$
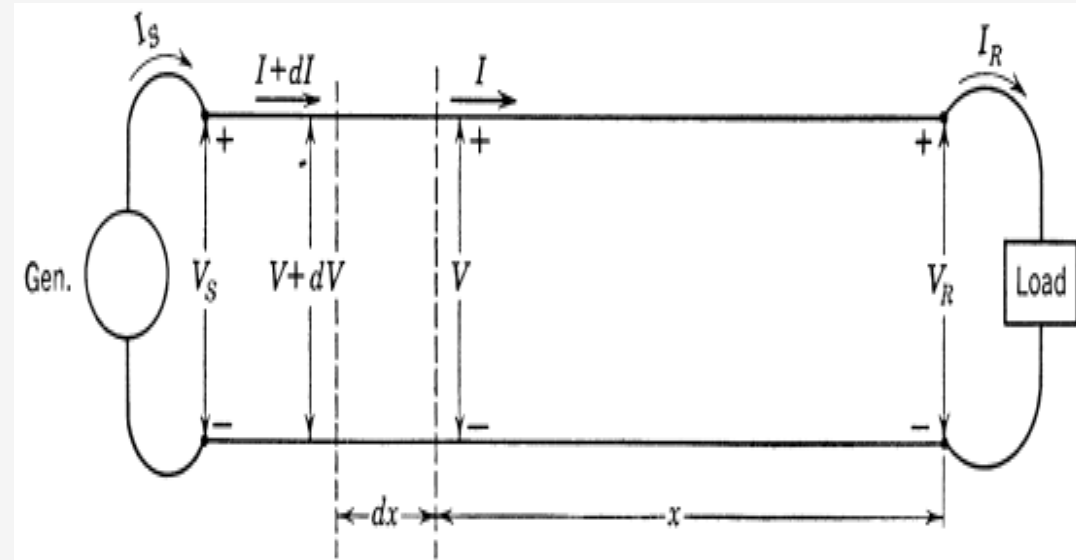
$$C = \frac{1}{Z_c} \sinh(\gamma l) \quad S$$



x : distance measured from the receiving end

EXAMPLE

A three-phase 765-kV, 60-Hz, 300-km, completely transposed line has the following positive-sequence impedance and admittance:

$$z = 0.0165 + j0.3306 = 0.3310 \angle 87.14^\circ \quad \Omega/\text{km}$$

$$y = j4.674 \times 10^{-6} \quad \text{S/km}$$

Assuming positive-sequence operation, calculate the exact $ABCD$ parameters of the line. Compare the exact B parameter with that of the nominal π circuit.

Solution

$$\begin{aligned} Z_c &= \sqrt{\frac{0.3310 \angle 87.14^\circ}{4.674 \times 10^{-6} \angle 90^\circ}} = \sqrt{7.082 \times 10^4 \angle -2.86^\circ} \\ &= 266.1 \angle -1.43^\circ \quad \Omega \end{aligned}$$

and

$$\begin{aligned} \gamma l &= \sqrt{(0.3310 \angle 87.14^\circ)(4.674 \times 10^{-6} \angle 90^\circ)} \times (300) \\ &= \sqrt{1.547 \times 10^{-6} \angle 177.14^\circ} \times (300) \\ &= 0.3731 \angle 88.57^\circ = 0.00931 + j0.3730 \quad \text{per unit} \end{aligned}$$

Solution

$$\begin{aligned}e^{\gamma l} &= e^{0.00931} e^{+j0.3730} = 1.0094/\underline{0.3730} \text{ radians} \\ &= 0.9400 + j0.3678\end{aligned}$$

and

$$\begin{aligned}e^{-\gamma l} &= e^{-0.00931} e^{-j0.3730} = 0.9907/\underline{-0.3730} \text{ radians} \\ &= 0.9226 - j0.3610\end{aligned}$$

$$\begin{aligned}\cosh(\gamma l) &= \frac{(0.9400 + j0.3678) + (0.9226 - j0.3610)}{2} \\ &= 0.9313 + j0.0034 = 0.9313/\underline{0.209^\circ}\end{aligned}$$

$$\begin{aligned}\sinh(\gamma l) &= \frac{(0.9400 + j0.3678) - (0.9226 - j0.3610)}{2} \\ &= 0.0087 + j0.3644 = 0.3645/\underline{88.63^\circ}\end{aligned}$$

Solution

$$A = D = \cosh(\gamma l) = 0.9313 \angle 0.209^\circ \quad \text{per unit}$$

$$B = (266.1 \angle -1.43^\circ)(0.3645 \angle 88.63^\circ) = 97.0 \angle 87.2^\circ \quad \Omega$$


$$C = \frac{0.3645 \angle 88.63^\circ}{266.1 \angle -1.43^\circ} = 1.37 \times 10^{-3} \angle 90.06^\circ \quad \text{S}$$

$$B_{\text{nominal } \pi} = Z = (0.3310 \angle 87.14^\circ)(300) = 99.3 \angle 87.14^\circ \quad \Omega$$

which is 2% larger than the exact value.

EQUIVALENT π CIRCUIT OF A LONG LINE

The nominal- π circuit do not represent a transmission line exactly because it does not account for the parameters of the line being uniformly distributed. The discrepancy between the nominal π and the actual line becomes larger as the length of line increases. It is possible, however, to find the equivalent circuit of a long transmission line and to represent the line accurately, in so far as measurements at the ends of the line are concerned, by a network of lumped parameters.

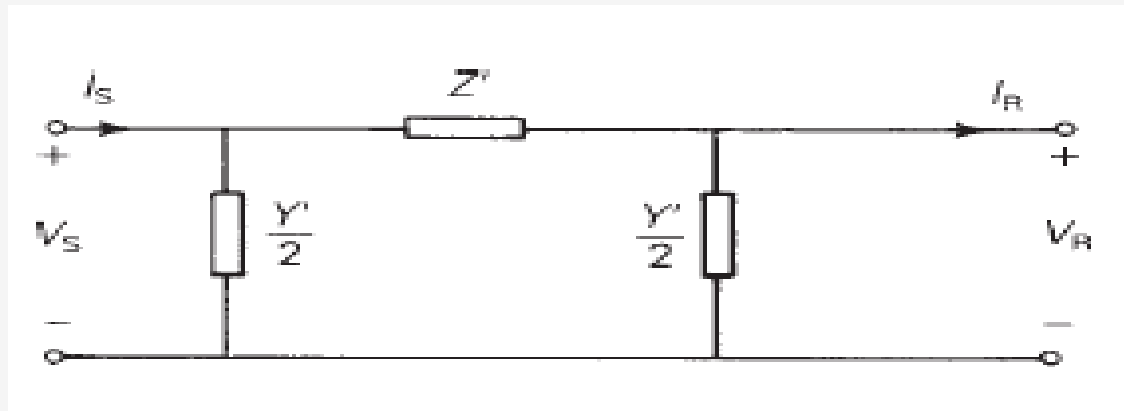

The circuit shown in Figure is called an equivalent π circuit. It is identical in structure to the nominal π circuit except that the series arm of our equivalent- π circuit Z' and the shunt arms $Y'/2$ to distinguish them from the arms of the nominal- π circuit.

Equivalent Circuit of a Long Line

$$V_S = \left(\frac{Z'Y'}{2} + 1 \right) V_R + Z' I_R$$

THEN,


$$V_S = V_R \cosh \gamma l + I_R Z_C \sinh \gamma l$$

$$Z' = Z_C \sinh \gamma l$$


$$Z' = \sqrt{\frac{z}{y}} \sinh \gamma l = zl \frac{\sinh \gamma l}{\sqrt{zy}l}$$

$$Z' = Z \frac{\sinh \gamma l}{\gamma l}$$

$Z = zl$ total series impedance

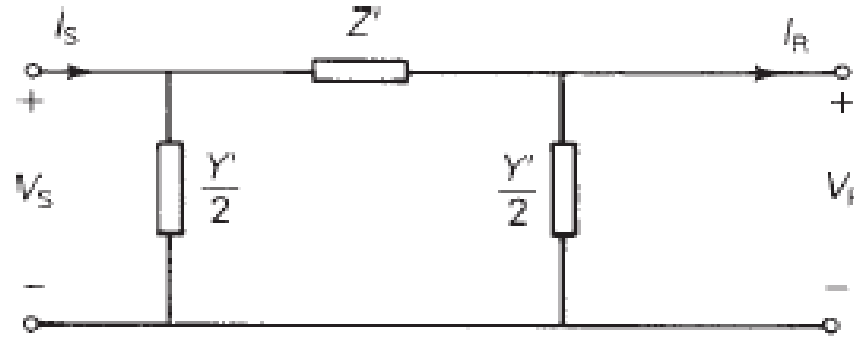

Equivalent - π Model

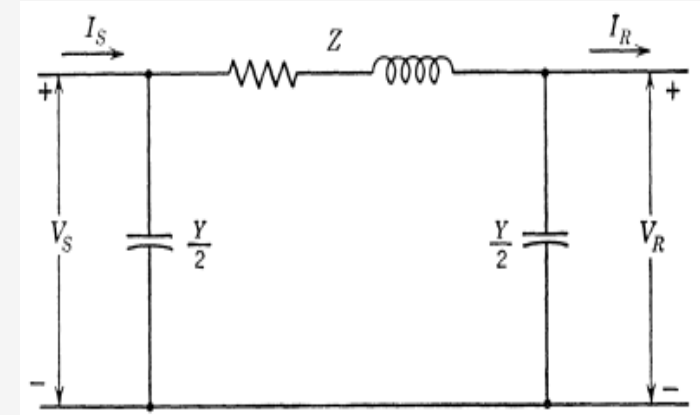

Nominal π Model

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} \left(1 + \frac{YZ}{2}\right) & Z \\ Y\left(1 + \frac{YZ}{4}\right) & \left(1 + \frac{YZ}{2}\right) \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

Equivalent Circuit of a Long Line


$(\sinh \gamma l)/\gamma l$ term is a correction factor to convert series impedance for the nominal π circuit to and series impedance for the equivalent π circuit.

In order to find the shunt admittance

$$A = \frac{Z'Y'}{2} + 1 = \cosh \gamma l$$

use $Z_C \sinh \gamma l$ instead of Z' then

$$\frac{Y'Z_C \sinh \gamma l}{2} + 1 = \cosh \gamma l$$

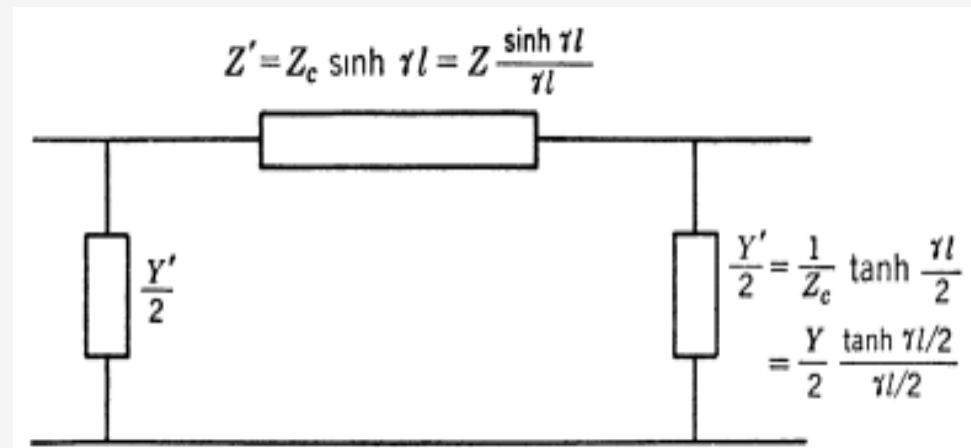

$$\frac{Y'}{2} = \frac{1}{Z_C} \frac{\cosh \gamma l - 1}{\sinh \gamma l}$$

o $\tanh \frac{\gamma l}{2} = \frac{\cosh \gamma l - 1}{\sinh \gamma l}$

Equivalent- π Circuit

$$\frac{Y'}{2} = \frac{\cosh(\gamma l) - 1}{Z_c \sinh(\gamma l)} = \frac{\tanh(\gamma l/2)}{Z_c} = \frac{\tanh(\gamma l/2)}{\sqrt{\frac{z}{y}}}$$


$$\frac{Y'}{2} = \frac{yl}{2} \left[\frac{\tanh(\gamma l/2)}{\sqrt{\frac{z}{y}} \frac{yl}{2}} \right] = \frac{yl}{2} \left[\frac{\tanh(\gamma l/2)}{\sqrt{zy} l/2} \right]$$




Correction Factors

$$F_1 = \frac{\sinh(\gamma l)}{\gamma l}$$
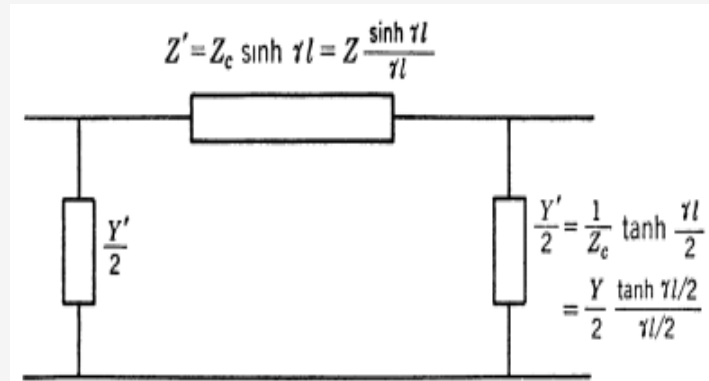
$$F_2 = \frac{\tanh(\gamma l/2)}{\gamma l/2}$$



Equivalent - π Model

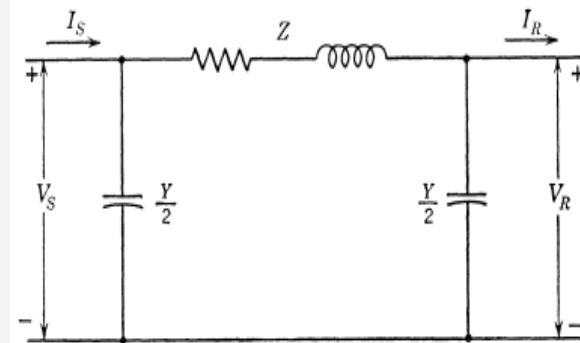

Nominal - π Model

EXAMPLE

A three-phase 765-kV, 60-Hz, 300-km, completely transposed line with

$$z = 0.0165 + j0.3306 = 0.3310/\underline{87.14^\circ} \quad \Omega/\text{km}$$

$$y = j4.674 \times 10^{-6} \quad \text{S/km}$$

Compare the equivalent and nominal π circuits for the line

SOLUTION For the nominal π circuit,

$$Z = zl = (0.3310/\underline{87.14^\circ})(300) = 99.3/\underline{87.14^\circ} \quad \Omega$$

$$\frac{Y}{2} = \frac{yl}{2} = \left(\frac{j4.674 \times 10^{-6}}{2} \right) (300) = 7.011 \times 10^{-4} \underline{90^\circ} \quad \text{S}$$

$$Z_c = \sqrt{\frac{0.3310 \angle 87.14^\circ}{4.674 \times 10^{-6} \angle 90^\circ}} = \sqrt{7.082 \times 10^4 \angle -2.86^\circ}$$

$$= 266.1 \angle -1.43^\circ \quad \Omega$$

and

$$\gamma l = \sqrt{(0.3310 \angle 87.14^\circ)(4.674 \times 10^{-6} \angle 90^\circ)} \times (300)$$

$$= \sqrt{1.547 \times 10^{-6} \angle 177.14^\circ} \times (300)$$

$$= 0.3731 \angle 88.57^\circ = 0.00931 + j0.3730 \quad \text{per unit}$$

$$e^{\gamma l} = e^{0.00931} e^{+j0.3730} = 1.0094 \angle 0.3730 \quad \text{radians}$$

$$= 0.9400 + j0.3678$$

and

$$e^{-\gamma l} = e^{-0.00931} e^{-j0.3730} = 0.9907 \angle -0.3730 \quad \text{radians}$$

$$= 0.9226 - j0.3610$$

$$\cosh(\gamma l) = \frac{(0.9400 + j0.3678) + (0.9226 - j0.3610)}{2}$$

$$= 0.9313 + j0.0034 = 0.9313 \angle 0.209^\circ$$

$$\sinh(\gamma l) = \frac{(0.9400 + j0.3678) - (0.9226 - j0.3610)}{2}$$

$$= 0.0087 + j0.3644 = 0.3645 \angle 88.63^\circ$$

Correction Factors

$$F_1 = \frac{\sinh(\gamma l)}{\gamma l}$$



$$F_1 = \frac{0.3645/\underline{88.63^\circ}}{0.3731/\underline{88.57^\circ}} = 0.9769/\underline{0.06^\circ} \quad \text{per unit}$$

$$\begin{aligned} F_2 &= \frac{\tanh(\gamma l/2)}{\gamma l/2} = \frac{\cosh(\gamma l) - 1}{(\gamma l/2) \sinh(\gamma l)} \\ &= \frac{0.9313 + j0.0034 - 1}{\left(\frac{0.3731}{2}/\underline{88.57^\circ}\right)(0.3645/\underline{88.63^\circ})} \\ &= \frac{-0.0687 + j0.0034}{0.06800/\underline{177.20^\circ}} \\ &= \frac{0.06878/\underline{177.17^\circ}}{0.06800/\underline{177.20^\circ}} = 1.012/\underline{-0.03^\circ} \quad \text{per unit} \end{aligned}$$

EXAMPLE

$$Z' = (99.3/\underline{87.14^\circ})(0.9769/\underline{0.06^\circ}) = 97.0/\underline{87.2^\circ} \quad \Omega$$

$$\begin{aligned}\frac{Y'}{2} &= (7.011 \times 10^{-4}/\underline{90^\circ})(1.012/\underline{-0.03^\circ}) = 7.095 \times 10^{-4}/\underline{89.97^\circ} \quad \text{S} \\ &= 3.7 \times 10^{-7} + j7.095 \times 10^{-4} \quad \text{S}\end{aligned}$$

Comparing these nominal and equivalent π circuit values, Z' is about 2% smaller than Z , and $Y'/2$ is about 1% larger than $Y/2$. Although the circuit values are approximately the same for this line, the equivalent π circuit should be used for accurate calculations involving long lines. Note the small shunt conductance. $G' = 3.7 \times 10^{-7} \text{ S}$. introduced in the equivalent π circuit.

TUTORIAL

3 Phase 60 Hz transmission line with $l = 230$ mil es. 125 MW is transferred to the receiving end at unity power factor. Receiving end voltage is 215 KV (line-line)

Line parameters are

$$z = 0.8431 \angle 79.04^\circ \Omega/\text{mi}$$

$$y = 5.105 \times 10^{-6} \angle 90^\circ \text{ S}/\text{mi}$$

Find the sending end voltage and current.

$$\begin{aligned} \gamma l &= \sqrt{yz} l = 230 \sqrt{0.8431 \times 5.105 \times 10^{-6}} \angle \frac{79.04^\circ + 90^\circ}{2} \\ &= 0.4772 \angle 84.52^\circ = 0.0456 + j0.4750 \end{aligned}$$

$$Z_c = \sqrt{\frac{z}{y}} = \sqrt{\frac{0.8431}{5.105 \times 10^{-6}}} \angle \frac{79.04^\circ - 90^\circ}{2} = 406.4 \angle -5.48^\circ \Omega$$

$$V_R = \frac{215,000}{\sqrt{3}} = 124,130 \angle 0^\circ \text{ V to neutral}$$

$$I_R = \frac{125,000,000}{\sqrt{3} \times 215,000} = 335.7 \angle 0^\circ \text{ A}$$

TUTORIAL

$$\cosh(\alpha + j\beta) = \frac{\varepsilon^{\alpha} \varepsilon^{j\beta} + \varepsilon^{-\alpha} \varepsilon^{-j\beta}}{2} = \frac{1}{2}(\varepsilon^{\alpha} \angle \beta + \varepsilon^{-\alpha} \angle -\beta)$$

$$\sinh(\alpha + j\beta) = \frac{\varepsilon^{\alpha} \varepsilon^{j\beta} - \varepsilon^{-\alpha} \varepsilon^{-j\beta}}{2} = \frac{1}{2}(\varepsilon^{\alpha} \angle \beta - \varepsilon^{-\alpha} \angle -\beta)$$

$$\cosh \gamma l = \frac{1}{2} \varepsilon^{0.0456} \angle 27.22^{\circ} + \frac{1}{2} \varepsilon^{-0.0456} \angle -27.22^{\circ}$$

$$= 0.4654 + j0.2394 + 0.4248 - j0.2185$$

$$= 0.8902 + j0.0209 = 0.8904 \angle 1.34^{\circ}$$

$$\sinh \gamma l = 0.4654 + j0.2394 - 0.4248 + j0.2185$$

$$= 0.0406 + j0.4579 = 0.4597 \angle 84.93^{\circ}$$

$$0.4750 \text{ rad} = 27.22^{\circ}$$

$$\begin{aligned} \text{ANGLE} &= 180 \times 0.475 / 3.14 \\ &= 27.22 \text{ degrees} \end{aligned}$$

TUTORIAL

$$V_S = V_R \cosh \gamma l + I_R Z_c \sinh \gamma l$$

$$I_S = I_R \cosh \gamma l + \frac{V_R}{Z_c} \sinh \gamma l$$

$$\begin{aligned} V_S &= 124,130 \times 0.8904 \angle 1.34^\circ + 335.7 \times 406.4 \angle -5.48^\circ \times 0.4597 \angle 84.93^\circ \\ &= 110,495 + j2,585 + 11,483 + j61,656 \\ &= 137,860 \angle 27.77^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} I_S &= 335.7 \times 0.8904 \angle 1.34^\circ + \frac{124,130}{406.4 \angle -5.48^\circ} \times 0.4597 \angle 84.93^\circ \\ &= 298.83 + j6.99 - 1.00 + j140.41 \\ &= 332.31 \angle 26.33^\circ \text{ A} \end{aligned}$$

$$V_S = \sqrt{3} \times 137.86 = 238.8 \text{ kV}$$